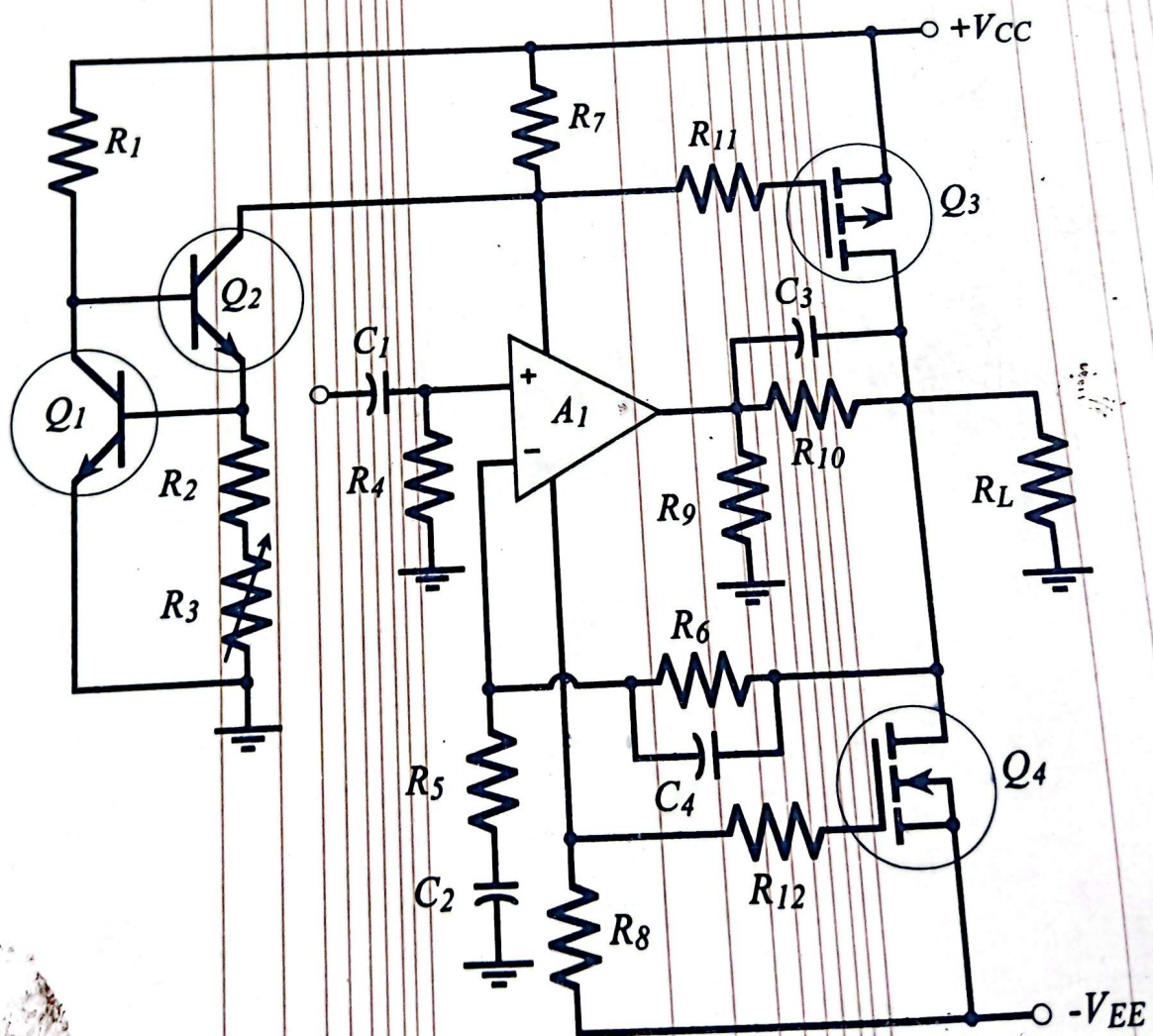


Fourth Edition

Electronic Devices and Circuits

11302

David A. Bell



Contents

Chapter 1 Basic Semiconductor and pn -Junction Theory 1

- Objectives 1
- Introduction 2
- 1-1 Atomic Theory 2
- 1-2 Conduction in Solids 5
- 1-3 Conductors, Semiconductors, and Insulators 7
- 1-4 n -Type and p -Type Semiconductors 9
- 1-5 The pn -Junction 12
- 1-6 Biased Junctions 14
- Review Questions 18

Chapter 2 Semiconductor Diodes 21

- Objectives 21
- Introduction 22
- 2-1 pn -Junction Diode 22
- 2-2 Characteristics and Parameters 23
- 2-3 Diode Approximations 26
- 2-4 DC Load Line Analysis 29
- 2-5 Temperature Effects 32
- 2-6 AC Equivalent Circuits 35
- 2-7 Diode Specifications 37
- 2-8 Diode Testing 39
- 2-9 Zener Diodes 41
- Review Questions 46
- Problems 47
- Practise Problem Answers 50

Chapter 3 Diode Applications 51

- Objectives 51
- Introduction 52
- 3-1 Half-Wave Rectification 52
- 3-2 Full-Wave Rectification 54
- 3-3 Half-Wave Rectifier DC Power Supply 57
- 3-4 Full-Wave Rectifier DC Power Supply 64
- 3-5 Power Supply Performance 68
- 3-6 Zener Diode Voltage Regulators 70
- 3-7 Series Clipping Circuits 74
- 3-8 Shunt Clipping Circuits 76
- 3-9 Clamping Circuits 80
- 3-10 DC Voltage Multipliers 86
- 3-11 Diode Logic Gates 90
- Review Questions 91
- Problems 93
- Practise Problem Answers 97

Chapter 4 Bipolar Junction Transistors 99

Objectives	99
Introduction	100
4-1 Transistor Operation	100
4-2 Transistor Voltages and Currents	104
4-3 Amplification	107
4-4 Common-Base Characteristics	109
4-5 Common-Emitter Characteristics	112
4-6 Common-Collector Characteristics	115
4-7 Transistor Testing	116
Review Questions	118
Problems	119
Practise Problem Answers	122

Chapter 5 BJT Biasing 123

Objectives	123
Introduction	124
5-1 DC Load Line and Bias Point	124
5-2 Base Bias Circuit	130
5-3 Collector-to-Base Bias	133
5-4 Voltage Divider Bias	136
5-5 Comparison of Basic Bias Circuits	142
5-6 Trouble-Shooting Bias Circuits	144
5-7 Bias Circuit Design	146
5-8 More Bias Circuits	151
5-9 Thermal Stability of Bias Circuits	155
5-10 Biasing Transistor Switching Circuits	160
Review Questions	165
Problems	167
Practise Problem Answers	172

Library Govt. College for Women
Serial No. 1130.2
Date _____ Initial _____

Chapter 6 AC Analysis of BJT Circuits 173

Objectives	173
Introduction	174
6-1 Coupling and Bypassing Capacitors	174
6-2 AC Load Lines	177
6-3 Transistor Models and Parameters	179
6-4 Common-Emitter Circuit Analysis	185
6-5 CE Circuit with Unbypassed Emitter Resistor	189
6-6 Common-Collector Circuit Analysis	192
6-7 Common-Base Circuit Analysis	196
6-8 Comparison of CE, CC, and CB Circuits	201
Review Questions	204
Problems	207
Practise Problem Answers	210

Chapter 7 Semiconductor Device and IC Fabrication 211

- Objectives 211
- Introduction 212
- 7-1 Processing of Semiconductor Material 212
- 7-2 Diode Fabrication and Packaging 213
- 7-3 Transistor Construction and Performance 215
- 7-4 Transistor Fabrication 216
- 7-5 Integrated Circuits 219
- 7-6 Integrated Circuit Components 220
- 7-7 Transistor and IC Packaging 222
- Review Questions 223

Chapter 8 Transistor Specifications and Performance 225

- Objectives 225
- Introduction 226
- 8-1 Transistor Data Sheets 226
- 8-2 Decibels and Frequency Response 229
- 8-3 BJT Cutoff Frequency and Capacitances 232
- 8-4 BJT Circuit Frequency Response 234
- 8-5 Transistor Switching Times 238
- 8-6 Transistor Circuit Noise 239
- 8-7 Transistor Power Dissipation 243
- 8-8 Heat Sinking 247
- Review Questions 250
- Problems 252
- Practise Problem Answers 254

Chapter 9 Field Effect Transistors 257

- Objectives 257
- Introduction 258
- 9-1 Junction Field Effect Transistors 258
- 9-2 JFET Characteristics 261
- 9-3 JFET Data Sheet and Parameters 267
- 9-4 FET Amplification 273
- 9-5 MOSFETs 275
- Review Questions 282
- Problems 283
- Practise Problem Answers 286

Chapter 10 FET Biasing 287

- Objectives 287
- Introduction 288
- 10-1 DC Load Line and Bias Point 288
- 10-2 Gate Bias 291
- 10-3 Self Bias 294
- 10-4 Voltage Divider Bias 297

10-5	Comparison of Basic <i>JFET</i> Bias Circuits	300
10-6	Trouble-Shooting <i>JFET</i> Bias Circuits	301
10-7	<i>JFET</i> Bias Circuit Design	304
10-8	More <i>JFET</i> Bias Circuits	310
10-9	Use of Universal Transfer Characteristic	315
10-10	<i>MOSFET</i> Biasing	318
10-11	Biasing <i>FET</i> Switching Circuits	322
	Review Questions	324
	Problems	327
	Practise Problem Answers	333

Chapter 11 AC Analysis of FET Circuits 335

	Objectives	335
	Introduction	336
11-1	Coupling, Bypassing, and AC Load Lines	336
11-2	<i>FET</i> Models and Parameters	338
11-3	Common Source Circuit Analysis	339
11-4	CS Circuit With Unbypassed Source Resistor	343
11-5	Common Drain Circuit Analysis	346
11-6	Common Gate Circuit Analysis	350
11-7	Comparison of <i>FET</i> and <i>BJT</i> Circuits	353
11-8	Frequency Response of <i>FET</i> Circuits	356
	Review Questions	358
	Problems	361
	Practise Problem Answers	364

Chapter 12 Small Signal Amplifiers 365

	Objectives	365
	Introduction	366
12-1	Single-Stage Common-Emitter Amplifier	366
12-2	Single-Stage Common-Source Amplifier	373
12-3	Capacitor-Coupled Two-Stage CE Amplifier	378
12-4	Direct-Coupled Two-Stage Circuits	382
12-5	Two-Stage Circuit with Emitter-Follower Output	387
12-6	DC Feedback Pair	390
12-7	<i>BIFET</i> Circuits	395
12-8	Differential Amplifier	399
12-9	Small-Signal High-Frequency Amplifiers	405
12-10	Amplifier Testing	409
	Review Questions	412
	Problems	415
	Practise Problem Answers	419

Chapter 13 Amplifiers with Negative Feedback 421

	Objectives	421
	Introduction	422
13-1	Series Voltage Negative Feedback	422
13-2	Two-Stage CE Amplifier with Series Voltage	

- Negative Feedback 428
- 13-3 More Amplifiers with Series Voltage Negative Feedback 434
- 13-4 Two-Stage Differential-Input Amplifier with Negative Feedback 437
- 13-5 Emitter-Current Feedback 443
- 13-6 Parallel Current Negative Feedback 449
- 13-7 Additional Effects of Negative Feedback 453
- Review Questions 458
- Problems 460
- Practise Problem Answers 463

Chapter 14 IC Operational Amplifiers and Basic Op-amp Circuits 465

- Objectives 465
- Introduction 466
- 14-1 Integrated Circuit Operational Amplifiers 466
- 14-2 Biasing Operational Amplifiers 468
- 14-3 Voltage Follower Circuits 471
- 14-4 Noninverting Amplifiers 475
- 14-5 Inverting Amplifiers 478
- 14-6 Summing Amplifier 481
- 14-7 Difference Amplifier 483
- 14-8 Instrumentation Amplifier 486
- 14-9 Voltage Level Detectors 489
- 14-10 Schmitt Trigger Circuits 492
- Review Questions 497
- Problems 500
- Practise Problem Answers 504

Chapter 15 Operational Amplifier Frequency Response and Compensation 505

- Objectives 505
- Introduction 506
- 15-1 Operational Amplifier Circuit Stability 506
- 15-2 Frequency Compensation Methods 511
- 15-3 Op-amp Circuit Bandwidth and Slew Rate 514
- 15-4 Stray Capacitance Effects 518
- 15-5 Load Capacitance Effects 520
- 15-6 Circuit Stability Precautions 523
- Review Questions 524
- Problems 525
- Practise Problem Answers 527

Chapter 16 Signal Generators 529

- Objectives 529
- Introduction 530
- 16-1 Phase Shift Oscillators 530
- 16-2 Colpitts Oscillators 534

16-3	Hartley Oscillators	538
16-4	Wein Bridge Oscillator	541
16-5	Oscillator Amplitude Stabilization	543
16-6	Square Wave Generator	548
16-7	Triangular Wave Generator	550
16-8	Oscillator Frequency Stabilization	553
	Review Questions	557
	Problems	559
	Practise Problem Answers	561

Chapter 17 Linear and Switching Voltage Regulators 563

Objectives	563
Introduction	564
17-1	Transistor Series Regulator 564
17-2	Improving Regulator Performance 569
17-3	Current Limiting 575
17-4	Op-amp Voltage Regulators 579
17-5	IC Linear Voltage Regulators 582
17-6	Switching Regulator Basics 586
17-7	Step-Down, Step-Up, and Inverting Converters 589
17-8	IC Controller for Switching Regulators 595
Review Questions	599
Problems	601
Practise Problem Answers	604

Chapter 18 Audio Power Amplifiers 605

Objectives	605
Introduction	606
18-1	Transformer-Coupled Class-A Amplifier 606
18-2	Transformer-Coupled Class-B and Class-AB Amplifiers 612
18-3	Transformer-Coupled Amplifier Design 617
18-4	Capacitor-Coupled and Direct-Coupled Output Stages 620
18-5	Modifications to Improve Amplifier Performance 626
18-6	BJT Power Amplifier with Differential Input Stage 631
18-7	Complementary MOSFET Common-Source Power Amplifier 635
18-8	BJT Power Amplifiers with Op-Amp Driver 639
18-9	MOSFET Power Amplifier with Op-Amp Driver Stage 645
18-10	Integrated Circuit Power Amplifiers 653
Review Questions	660
Problems	663
Practise Problem Answers	668

Chapter 19 Thyristors 669

Objectives	669
Introduction	610
19-1	Silicon Controlled Rectifier (SCR) 670
19-2	SCR Control Circuits 675

19-3	More SCR Applications	681
19-4	TRIAC and DIAC	685
19-5	TRIAC Control Circuits	688
19-6	SUS, SBS, GTO, and SIDAC	692
19-7	Unijunction Transistor (UJT)	696
19-8	Programmable Unijunction Transistor (PUT)	703
	Review Questions	707
	Problems	709
	Practise Problem Answers	712

Chapter 20 Optoelectronic Devices 713

	Objectives	713
	Introduction	714
20-1	Light Units	714
20-2	Light Emitting Diode (LED)	716
20-3	Seven-Segment Displays	719
20-4	Photoconductive Cell	722
20-5	Photodiode and Solar Cell	727
20-6	Phototransistors	732
20-7	Optocouplers	735
	Review Questions	738
	Problems	740
	Practise Problem Answers	743

Chapter 21 Miscellaneous Devices 745

	Objectives	745
	Introduction	746
21-1	Voltage-Variable Capacitor Diodes	746
21-2	Thermistors	749
21-3	Tunnel Diodes	752
	Review Questions	758
	Problems	759
	Practise Problem Answers	760

Appendices 761

1	Device Data Sheets	762
2	Standard Component Values	784
3	Answers for Odd-Numbered Problems	787

Index 791