

**CAMBRIDGE
LOW PRICE
EDITIONS**

Second edition

The art of electronics

**Paul Horowitz
Winfield Hill**

11315

CONTENTS

List of tables xvi

Preface xix

Preface to first edition xxi

CHAPTER 1 FOUNDATIONS 1

Introduction 1

Voltage, current, and resistance 2

1.01 Voltage and current 2

1.02 Relationship between voltage and current: resistors 4

1.03 Voltage dividers 8

1.04 Voltage and current sources 9

1.05 Thévenin's equivalent circuit 11

1.06 Small-signal resistance 13

Signals 15

1.07 Sinusoidal signals 15

1.08 Signal amplitudes and decibels 16

1.09 Other signals 17

1.10 Logic levels 19

1.11 Signal sources 19

Capacitors and ac circuits 20

1.12 Capacitors 20

1.13 RC circuits: V and I versus time 23

1.14 Differentiators 25

1.15 Integrators 26

Inductors and transformers 28

1.16 Inductors 28

1.17 Transformers 28

Impedance and reactance 29

1.18 Frequency analysis of reactive circuits 30

1.19 RC filters 35

1.20 Phasor diagrams 39

1.21 "Poles" and decibels per octave 40

1.22 Resonant circuits and active filters 41

1.23 Other capacitor applications 42

1.24 Thévenin's theorem generalized 44

Diodes and diode circuits 44

1.25 Diodes 44

1.26 Rectification 44

1.27 Power-supply filtering 45

1.28 Rectifier configurations for power supplies 46

1.29 Regulators 48

1.30 Circuit applications of diodes 48

1.31 Inductive loads and diode protection 52

Other passive components 53

1.32 Electromechanical devices 53

1.33 Indicators 57

1.34 Variable components 57

Additional exercises 58

CHAPTER 2 TRANSISTORS 61

Introduction 61

2.01 First transistor model: current amplifier 62

Some basic transistor circuits 63

2.02 Transistor switch 63

2.03 Emitter follower 65

- 2.04 Emitter followers as voltage regulators 68
- 2.05 Emitter follower biasing 69
- 2.06 Transistor current source 72
- 2.07 Common-emitter amplifier 76
- 2.08 Unity-gain phase splitter 77
- 2.09 Transconductance 78

Ebers-Moll model applied to basic transistor circuits 79

- 2.10 Improved transistor model: transconductance amplifier 79
- 2.11 The emitter follower revisited 81
- 2.12 The common-emitter amplifier revisited 82
- 2.13 Biasing the common-emitter amplifier 84
- 2.14 Current mirrors 88

Some amplifier building blocks 91

- 2.15 Push-pull output stages 91
- 2.16 Darlington connection 94
- 2.17 Bootstrapping 96
- 2.18 Differential amplifiers 98
- 2.19 Capacitance and Miller effect 102
- 2.20 Field-effect transistors 104

Some typical transistor circuits 104

- 2.21 Regulated power supply 104
- 2.22 Temperature controller 105
- 2.23 Simple logic with transistors and diodes 107

Self-explanatory circuits 107

- 2.24 Good circuits 107
- 2.25 Bad circuits 107
- Additional exercises 107

CHAPTER 3 FIELD-EFFECT TRANSISTORS 113

Introduction 113

- 3.01 FET characteristics 114
- 3.02 FET types 117
- 3.03 Universal FET characteristics 119
- 3.04 FET drain characteristics 121
- 3.05 Manufacturing spread of FET characteristics 122

Basic FET circuits 124

- 3.06 JFET current sources 125
- 3.07 FET amplifiers 129
- 3.08 Source followers 133
- 3.09 FET gate current 135
- 3.10 FETs as variable resistors 138

FET switches 140

- 3.11 FET analog switches 141
- 3.12 Limitations of FET switches 144
- 3.13 Some FET analog switch examples 151
- 3.14 MOSFET logic and power switches 153
- 3.15 MOSFET handling precautions 169

Self-explanatory circuits 171

- 3.16 Circuit ideas 171
- 3.17 Bad circuits 171 vskip6pt

CHAPTER 4 FEEDBACK AND OPERATIONAL AMPLIFIERS 175

Introduction 175

- 4.01 Introduction to feedback 175
- 4.02 Operational amplifiers 176
- 4.03 The golden rules 177

Basic op-amp circuits 177

- 4.04 Inverting amplifier 177
- 4.05 Noninverting amplifier 178
- 4.06 Follower 179
- 4.07 Current sources 180
- 4.08 Basic cautions for op-amp circuits 182

An op-amp smorgasbord 183

- 4.09 Linear circuits 183
- 4.10 Nonlinear circuits 187

A detailed look at op-amp behavior 188

- 4.11 Departure from ideal op-amp performance 189
- 4.12 Effects of op-amp limitations on circuit behavior 193
- 4.13 Low-power and programmable op-amps 210

A detailed look at selected op-amp circuits 213

4.14 Logarithmic amplifier 213

4.15 Active peak detector 217

4.16 Sample-and-hold 220

4.17 Active clamp 221

4.18 Absolute-value circuit 221

4.19 Integrators 222

4.20 Differentiators 224

Op-amp operation with a single power supply 224

4.21 Biasing single-supply ac amplifiers 225

4.22 Single-supply op-amps 225

Comparators and Schmitt trigger 229

4.23 Comparators 229

4.24 Schmitt trigger 231

Feedback with finite-gain amplifiers 232

4.25 Gain equation 232

4.26 Effects of feedback on amplifier circuits 233

4.27 Two examples of transistor amplifiers with feedback 236

Some typical op-amp circuits 238

4.28 General-purpose lab amplifier 238

4.29 Voltage-controlled oscillator 240

4.30 JFET linear switch with R_{ON} compensation 241

4.31 TTL zero-crossing detector 242

4.32 Load-current-sensing circuit 242

Feedback amplifier frequency compensation 242

4.33 Gain and phase shift versus frequency 243

4.34 Amplifier compensation methods 245

4.35 Frequency response of the feedback network 247

Self-explanatory circuits 250

4.36 Circuit ideas 250

4.37 Bad circuits 250

Additional exercises 251

CHAPTER 5

ACTIVE FILTERS AND OSCILLATORS 263

Active filters 263

5.01 Frequency response with RC filters 263

5.02 Ideal performance with LC filters 265

5.03 Enter active filters: an overview 266

5.04 Key filter performance criteria 267

5.05 Filter types 268

Active filter circuits 272

5.06 VCVS circuits 273

5.07 VCVS filter design using our simplified table 274

5.08 State-variable filters 276

5.09 Twin-T notch filters 279

5.10 Gyrator filter realizations 281

5.11 Switched-capacitor filters 281

Oscillators 284

5.12 Introduction to oscillators 284

5.13 Relaxation oscillators 284

5.14 The classic timer chip: the 555 286

5.15 Voltage-controlled oscillators 291

5.16 Quadrature oscillators 291

5.17 Wien bridge and LC oscillators 296

5.18 LC oscillators 297

5.19 Quartz-crystal oscillators 300

Self-explanatory circuits 303

5.20 Circuit ideas 303

Additional exercises 303

CHAPTER 6

VOLTAGE REGULATORS AND POWER CIRCUITS 307

Basic regulator circuits with the classic 723 307

6.01 The 723 regulator	307
6.02 Positive regulator	309
6.03 High-current regulator	311
Heat and power design	312
6.04 Power transistors and heat sinking	312
6.05 Foldback current limiting	316
6.06 Overvoltage crowbars	317
6.07 Further considerations in high-current power-supply design	320
6.08 Programmable supplies	321
6.09 Power-supply circuit example	323
6.10 Other regulator ICs	325
The unregulated supply	325
6.11 ac line components	326
6.12 Transformer	328
6.13 dc components	329
Voltage references	331
6.14 Zener diodes	332
6.15 Bandgap (V_{BE}) reference	335
Three-terminal and four-terminal regulators	341
6.16 Three-terminal regulators	341
6.17 Three-terminal adjustable regulators	344
6.18 Additional comments about 3-terminal regulators	345
6.19 Switching regulators and dc-dc converters	355
Special-purpose power-supply circuits	368
6.20 High-voltage regulators	368
6.21 Low-noise, low-drift supplies	374
6.22 Micropower regulators	376
6.23 Flying-capacitor (charge pump) voltage converters	377
6.24 Constant-current supplies	379
6.25 Commercial power-supply modules	382
Self-explanatory circuits	384
6.26 Circuit ideas	384
6.27 Bad circuits	384
Additional exercises	384

CHAPTER 7

PRECISION CIRCUITS AND LOW-NOISE TECHNIQUES 391

Precision op-amp design techniques 391

- 7.01 Precision versus dynamic range 391
- 7.02 Error budget 392
- 7.03 Example circuit: precision amplifier with automatic null offset 392
- 7.04 A precision-design error budget 394
- 7.05 Component errors 395
- 7.06 Amplifier input errors 396
- 7.07 Amplifier output errors 403
- 7.08 Auto-zeroing (chopper-stabilized) amplifiers 415

Differential and instrumentation amplifiers 421

- 7.09 Differencing amplifier 421
- 7.10 Standard three-op-amp instrumentation amplifier 425

Amplifier noise 428

- 7.11 Origins and kinds of noise 430
- 7.12 Signal-to-noise ratio and noise figure 433
- 7.13 Transistor amplifier voltage and current noise 436
- 7.14 Low-noise design with transistors 438
- 7.15 FET noise 443
- 7.16 Selecting low-noise transistors 445
- 7.17 Noise in differential and feedback amplifiers 445

Noise measurements and noise sources 449

- 7.18 Measurement without a noise source 449
- 7.19 Measurement with noise source 450
- 7.20 Noise and signal sources 452
- 7.21 Bandwidth limiting and rms voltage measurement 453
- 7.22 Noise potpourri 454

Interferer
grounding

7.23 In
7.24 Sig
7.25 Gr
ins

Self-exp

7.26 Ci
Addition

CHAPTER 8

DIGITAL

Basic lo

8.01 Di
8.02 Lo
8.03 Nu
8.04 Ga
8.05 Di
8.06 Ga
8.07 Ass

TTL and

8.08 Ca
8.09 IC
8.10 TT
cha
8.11 Thr
dev

Combina

8.12 Log
8.13 Min
map
8.14 Cor
as I
8.15 Imp
tabl

Sequentia

8.16 Dev
flops
8.17 Clo
8.18 Com
sequ
8.19 Sync

Interference: shielding and grounding 455

- 7.23 Interference 455
- 7.24 Signal grounds 457
- 7.25 Grounding between instruments 457

Self-explanatory circuits 466

- 7.26 Circuit ideas 466
- Additional exercises* 466

CHAPTER 8 DIGITAL ELECTRONICS 471

Basic logic concepts 471

- 8.01 Digital versus analog 471
- 8.02 Logic states 472
- 8.03 Number codes 473
- 8.04 Gates and truth tables 478
- 8.05 Discrete circuits for gates 480
- 8.06 Gate circuit example 481
- 8.07 Assertion-level logic notation 482

TTL and CMOS 484

- 8.08 Catalog of common gates 484
- 8.09 IC gate circuits 485
- 8.10 TTL and CMOS characteristics 486
- 8.11 Three-state and open-collector devices 487

Combinational logic 490

- 8.12 Logic identities 491
- 8.13 Minimization and Karnaugh maps 492
- 8.14 Combinational functions available as ICs 493
- 8.15 Implementing arbitrary truth tables 500

Sequential logic 504

- 8.16 Devices with memory: flip-flops 504
- 8.17 Clocked flip-flops 507
- 8.18 Combining memory and gates: sequential logic 512
- 8.19 Synchronizer 515

Monostable multivibrators 517

- 8.20 One-shot characteristics 517
- 8.21 Monostable circuit example 519
- 8.22 Cautionary notes about monostables 519
- 8.23 Timing with counters 522

Sequential functions available as ICs 523

- 8.24 Latches and registers 523
- 8.25 Counters 524
- 8.26 Shift registers 525
- 8.27 Sequential PALs 527
- 8.28 Miscellaneous sequential functions 541

Some typical digital circuits 544

- 8.29 Modulo- n counter: a timing example 544
- 8.30 Multiplexed LED digital display 546
- 8.31 Sidereal telescope drive 548
- 8.32 An n -pulse generator 548

Logic pathology 551

- 8.33 dc problems 551
- 8.34 Switching problems 552
- 8.35 Congenital weaknesses of TTL and CMOS 554

Self-explanatory circuits 556

- 8.36 Circuit ideas 556
- 8.37 Bad circuits 556
- Additional exercises* 556

CHAPTER 9 DIGITAL MEETS ANALOG 565

CMOS and TTL logic interfacing 565

- 9.01 Logic family chronology 565
- 9.02 Input and output characteristics 570
- 9.03 Interfacing between logic families 572
- 9.04 Driving CMOS and TTL inputs 575
- 9.05 Driving digital logic from comparators and op-amps 577

9.06	Some comments about logic inputs	579
9.07	Comparators	580
9.08	Driving external digital loads from CMOS and TTL	582
9.09	NMOS LSI interfacing	588
9.10	Opto-electronics	590
	Digital signals and long wires	599
9.11	On-board interconnections	599
9.12	Inter-card connections	601
9.13	Data buses	602
9.14	Driving cables	603
	Analog/digital conversion	612
9.15	Introduction to A/D conversion	612
9.16	Digital-to-analog converters (DACs)	614
9.17	Time-domain (averaging) DACs	618
9.18	Multiplying DACs	619
9.19	Choosing a DAC	619
9.20	Analog-to-digital converters	621
9.21	Charge-balancing techniques	626
9.22	Some unusual A/D and D/A converters	630
9.23	Choosing an ADC	631
	Some A/D conversion examples	636
9.24	16-Channel A/D data-acquisition system	636
9.25	$3\frac{1}{2}$ -Digit voltmeter	638
9.26	Coulomb meter	640
	Phase-locked loops	641
9.27	Introduction to phase-locked loops	641
9.28	PLL design	646
9.29	Design example: frequency multiplier	647
9.30	PLL capture and lock	651
9.31	Some PLL applications	652
	Pseudo-random bit sequences and noise generation	655
	Feedback shift register sequences	655

9.33	Feedback shift register sequences	655
9.34	Analog noise generation from maximal-length sequences	659
9.35	Power spectrum of shift register sequences	658
9.36	Low-pass filtering	660
9.37	Wrap-up	661
9.38	Digital filters	664
	Self-explanatory circuits	667
9.39	Circuit ideas	667
9.40	Bad circuits	668
	Additional exercises	668

CHAPTER 10 MICROCOMPUTERS 673

Minicomputers, microcomputers, and microprocessors 673

10.01 Computer architecture 674

A computer instruction set 678

10.02 Assembly language and machine language 678

10.03 Simplified 8086/8 instruction set 679

10.04 A programming example 683

Bus signals and interfacing 684

10.05 Fundamental bus signals: data, address, strobe 684

10.06 Programmed I/O: data out 685

10.07 Programmed I/O: data in 689

10.08 Programmed I/O: status registers 690

10.09 Interrupts 693

10.10 Interrupt handling 695

10.11 Interrupts in general 701

10.12 Direct memory access 701

10.13 Summary of the IBM PC's bus signals 704

10.14 Synchronous versus asynchronous bus communication 707

10.15 Other microcomputer buses 709

10.16 Connecting peripherals to the computer 711

Software sys

10.17 Progra

10.18 Opera
memo

Data commu

10.19 Serial
ASCI

10.20 Paralle
Centr
GP

10.21 Local

10.22 Interf
packi

10.23 Num

CHAPTER
MICROPRO

A detailed i

11.01 Regi

11.02 Instr
addr

11.03 Mac
repe

11.04 Bus

A complete
signal aver

11.05 Circ

11.06 Prog
task

11.07 Prog

11.08 Perf

11.09 Som

Microproce

11.10 Med

11.11 Peri

11.12 Men

11.13 Oth

11.14 Emu
logic
boar

Software system concepts	714
10.17 Programming	714
10.18 Operating systems, files, and use of memory	716

Data communications concepts	719
10.19 Serial communication and ASCII	720
10.20 Parallel communication: Centronics, SCSI, IPI, GPIB (488)	730
10.21 Local area networks	734
10.22 Interface example: hardware data packing	736
10.23 Number formats	738

CHAPTER 11 MICROPROCESSORS 743

A detailed look at the 68008	744
11.01 Registers, memory, and I/O	744
11.02 Instruction set and addressing	745
11.03 Machine-language representation	750
11.04 Bus signals	753

A complete design example: analog signal averager 760

11.05 Circuit design	760
11.06 Programming: defining the task	774
11.07 Programming: details	777
11.08 Performance	796
11.09 Some afterthoughts	797

Microprocessor support chips 799

11.10 Medium-scale integration	800
11.11 Peripheral LSI chips	802
11.12 Memory	812
11.13 Other microprocessors	820
11.14 Emulators, development systems, logic analyzers, and evaluation boards	821

CHAPTER 12 ELECTRONIC CONSTRUCTION TECHNIQUES 827

Prototyping methods 827

12.01 Breadboards	827
12.02 PC prototyping boards	828
12.03 Wire-Wrap panels	828

Printed circuits 830

12.04 PC board fabrication	830
12.05 PC board design	835
12.06 Stuffing PC boards	838
12.07 Some further thoughts on PC boards	840
12.08 Advanced techniques	841

Instrument construction 852

12.09 Housing circuit boards in an instrument	852
12.10 Cabinets	854
12.11 Construction hints	855
12.12 Cooling	855
12.13 Some electrical hints	858
12.14 Where to get components	860

CHAPTER 13 HIGH-FREQUENCY AND HIGH-SPEED TECHNIQUES 863

High-frequency amplifiers 863

13.01 Transistor amplifiers at high frequencies: first look	863
13.02 High-frequency amplifiers: the ac model	864
13.03 A high-frequency calculation example	866
13.04 High-frequency amplifier configurations	868
13.05 A wideband design example	869
13.06 Some refinements to the ac model	872
13.07 The shunt-series pair	872
13.08 Modular amplifiers	873

Radiofrequency circuit elements 879

13.09 Transmission lines	879
--------------------------	-----

13.10 Stubs, baluns, and transformers 881

13.11 Tuned amplifiers 882

13.12 Radiofrequency circuit elements 884

13.13 Measuring amplitude or power 888

Radiofrequency communications:
AM 892

13.14 Some communications concepts 892

13.15 Amplitude modulation 894

13.16 Superheterodyne receiver 895

Advanced modulation methods 897

13.17 Single sideband 897

13.18 Frequency modulation 898

13.19 Frequency-shift keying 900

13.20 Pulse-modulation schemes 900

Radiofrequency circuit tricks 902

13.21 Special construction techniques 902

13.22 Exotic RF amplifiers and devices 903

High-speed switching 904

13.23 Transistor model and equations 905

13.24 Analog modeling tools 908

Some switching-speed examples 909

13.25 High-voltage driver 909

13.26 Open-collector bus driver 910

13.27 Example: photomultiplier preamp 911

Self-explanatory circuits 913

13.28 Circuit ideas 913

Additional exercises 913

CHAPTER 14

LOW-POWER DESIGN 917

Introduction 917

14.01 Low-power applications 918

Power sources 920

14.02 Battery types 920

14.03 Wall-plug-in units 931

14.04 Solar cells 932

14.05 Signal currents 933

Power switching and micropower regulators 938

14.06 Power switching 938

14.07 Micropower regulators 941

14.08 Ground reference 944

14.09 Micropower voltage references and temperature sensors 948

Linear micropower design techniques 948

14.10 Problems of micropower linear design 950

14.11 Discrete linear design example 950

14.12 Micropower operational amplifiers 951

14.13 Micropower comparators 965

14.14 Micropower timers and oscillators 965

Micropower digital design 969

14.15 CMOS families 969

14.16 Keeping CMOS low power 970

14.17 Micropower microprocessors and peripherals 974

14.18 Microprocessor design example: degree-day logger 978

Self-explanatory circuits 985

14.19 Circuit ideas 985

CHAPTER 15 MEASUREMENTS AND SIGNAL PROCESSING 987

Overview 987

Measurement transducers 988

15.01 Temperature 988

15.02 Light level 996

15.03 Strain and displacement 1001

15.04 Acceleration
velocity

15.05 Magnetic

15.06 Vacuum

15.07 Particles

15.08 Biological
probe

Precision signal
measurements

15.09 Frequency

15.10 Frequency
interference

15.11 Voltage
and current

Bandwidth

15.12 The
ratio

15.13 Signal
averaging

15.14 Malfunction

15.15 Location

15.16 Pulse

15.17 Timing
103

Spectrum
transform

15.18 Spectral
15.19 Offset

Self-explanatory

15.20 Circuit

- 15.04 Acceleration, pressure, force, velocity 1004
- 15.05 Magnetic field 1007
- 15.06 Vacuum gauges 1007
- 15.07 Particle detectors 1008
- 15.08 Biological and chemical voltage probes 1012

Precision standards and precision measurements 1016

- 15.09 Frequency standards 1016
- 15.10 Frequency, period, and time-interval measurements 1019
- 15.11 Voltage and resistance standards and measurements 1025

Bandwidth-narrowing techniques 1026

- 15.12 The problem of signal-to-noise ratio 1026
- 15.13 Signal averaging and multichannel averaging 1026
- 15.14 Making a signal periodic 1030
- 15.15 Lock-in detection 1031
- 15.16 Pulse-height analysis 1034
- 15.17 Time-to-amplitude converters 1035

Spectrum analysis and Fourier transforms 1035

- 15.18 Spectrum analyzers 1035
- 15.19 Off-line spectrum analysis 1038

Self-explanatory circuits 1038

- 15.20 Circuit ideas 1038

APPENDIXES 1043

Appendix A

The oscilloscope 1045

Appendix B

Math review 1050

Appendix C

The 5% resistor color code 1053

Appendix D

1% Precision resistors 1054

Appendix E

How to draw schematic diagrams 1056

Appendix F

Load lines 1059

Appendix G

Transistor saturation 1062

Appendix H

LC Butterworth filters 1064

Appendix I

Electronics magazines and journals 1068

Appendix J

IC prefixes 1069

Appendix K

Data sheets 1072

2N4400-1 NPN transistor 1073

LF411-12 JFET operational

amplifier 1078

LM317 3-terminal adjustable

regulator 1086

Bibliography 1095

Index 1101