

**CAMBRIDGE
LOW PRICE
EDITIONS**

Student manual for

The art of electronics

**Thomas C. Hayes
Paul Horowitz**

11316

Contents

ANALOG

Chapter 1: Foundations

Overview: Chapter 1	1
Class 1: DC Circuits	3
Worked example: Resistors & instruments	15
Lab 1: DC circuits	24

Class 2: Capacitors & RC Circuits	32
Worked example: RC circuits	46
A Note on reading capacitor values	51
Lab 2: Capacitors	54

Class 3: Diode Circuits	61
Worked example: Power supply	71
Lab 3: Diode circuits	75
Wrap-up: Ch. 1: Review	80
Jargon and terms	81

Chapter 2: Transistors (bipolar)

Overview: Chapters 2 & 3	82
Class 4: Transistors I: First Model	84
Worked example: Emitter follower	90
Lab 4: Transistors I	94

Class 5: Transistors II: Corrections to the first model: Ebers-Moll: r_e ; applying this new view	100
Worked example: Common-emitter amplifier (bypassed emitter)	115
Lab 5: Transistors II	118

Class 6: Transistors III: Differential amplifier; Miller effect	124
Worked example: Differential amplifier	131
Lab 6: Transistors III	134
Wrap-up Ch. 2: Review	139
Jargon and terms	140

Chapter 3: Field Effect Transistors

Class 7: FETs I (linear applications)	142
Worked example: Current source, source follower	153
Lab 7: FETs I (linear)	156
(We return to FETs in Lab 11)	

Chapter 4: Feedback and Operational Amplifiers

Overview: Feedback: Chapters 4, 5 & 6	163
Class 8: Op Amps I: Idealized view	166
Worked Example: Inverting amplifier; summing circuit	175
Lab 8: Op amps I	175

Class 9: Op Amps II: Departures from ideal	184
Worked example: Integrators; effects of op amp errors	196
Lab 9: Op amps II	200

Chapter 4 (continued); Chapter 5 Active Filters & Oscillators

Class 10: Op Amps III: Positive Feedback, Good and Bad: comparators, oscillators, and unstable circuits; a quantitative view of the effects of negative feedback	207
Appendix: Notes on op amp frequency compensation	222
Worked example: Effects of feedback (quantitative)	224
Schmitt trigger	227
Op Amp Innards: Annotated schematic of the LF411	232
Lab 10: Positive feedback, good and bad	233
Wrap-up Chs. 4 & 5: Review	242
Jargon and terms	243

Chapter 3: Field Effect Transistors (revisited)

Class 11: FETs II: Switches (power switching and analog switch applications)	244
Worked example: Sample and hold	250
Lab 11: FET switches	255
Wrap-up Ch. 3: Review	264
Jargon and terms	265

Chapter 6: Voltage Regulators and Power Circuits

Class 12: Voltage Regulators	267
Lab 12: Voltage regulators	274
Wrap-up Ch. 6: Jargon and terms	280

(This course omits the Text's *Chapter 7: Precision Circuits & Low-Noise Techniques*)

DIGITAL

Chapter 8: Digital Electronics

Overview: Chapters 8 & 9	281
Class 13: Digital Gates; Combinational Logic	281
Worked example: Multiplexers	283
Binary arithmetic	295
Lab 13: Digital gates	309

Class 14: Sequential Circuits: Flip-Flops	320
Worked example: combinational logic	332
Lab 14: Flip-flops	334

Class 15: Counters	342
Worked example: counter applications	351
Lab 15: Counters	362

Class 16: Memory; Buses; State Machines	375
Worked example: state machines	384
Lab 16: Memory; State Machines	394
Wrap-up Ch. 8: Review	403
Jargon and terms	404

Chapter 9: Digital Meets Analog

Class 17: Analog $\longleftrightarrow$ Digital; Phase-Locked Loop	406
Lab 17: Analog $\longleftrightarrow$ Digital; Phase-Locked Loop	421
Wrap-up Ch. 9: Review	430
Jargon and terms	430

Chapters 10, 11: Microcomputers; Microprocessors

Overview: Chapters 10 & 11	431
Class 18: μ 1: IBM PC and our lab microcomputer	433
Worked example: minimal 68008 controller	441
Lab 18: Add CPU	443

Class 19: Assembly Language; Inside the CPU; I/O Decoding	455
Supplementary notes: introduction to assembly language	467
Lab 19: μ 2: I/O	471

Class 20: μ 3: A/D $\longleftrightarrow$ D/A Interfacing; Masks; Data tables	479
Lab 20: Subroutines; More I/O Programming	489

Class 21: μ 4: More Assembly-Language Programming; 12-bit port	498
Worked example: 10 tiny programs	503
Worked Example: 12-bit frequency counter	518
Hand assembly: table of codes	521
Lab 21: A/D, D/A, Data Handling	525

Class 22: μ 5: Interrupts & Other 'Exceptions'	535
Debugging aid: Register Check in two forms	541
Lab 22: 'Storage scope'; Interrupts & other 'exceptions'	548

Class 23: μ 6: Wrap-up: Buying and Building	562
Lab 23: Applying your microcomputer ('Toy Catalog')	567
Wrap-up Chapters 10, 11: Review	586
Jargon and terms	587

Appendix:

A Equipment and Parts List	588
B Selected data sheets	
2N5485 JFET	592
DG403 analog switch	593
74HC74 dual D FLIP-FLOP	595
AD7569 8-bit A/D, D/A	597
68008 execution times and timing diagram	600
25120 write-only memory	605
C Big Picture: Schematic of lab microcomputer	606
D Pinouts	608

Index	612
-------	-----